

## Table of Contents

- Lab 4: Introduction to Sequential Logic - Latches and Flip Flops - pg. 2
  - Lab 4-1: S/R and D Latches - pg. 3
  - Lab 4-2: Gated or Clocked Latches - pg. 5
  - Lab 4-3: Toggle Flip Flops - pg. 8
  - Lab 4-4: J/K Flip Flops - pg. 14
- Lab 5: Digital Counters and Shift Registers - pg. 23
  - Lab 5-1: Asynchronous Counters - pg. 29
  - Lab 5-2: Synchronous Counters - pg. 32
  - Lab 5-3: Ring Counters and Shift Registers - pg. 42
- Lab 6: Clocks, Converters, Sensors, Isolation, and Drivers - pg. 51
  - Lab 6-1: Clock Sources - pg. 52
  - Lab 6-2: Chicken Coop Heater - pg. 66
  - Lab 6-3: DC Motor Controller / Drivers - pg. 72
- Lab 7: Project - Heart Rate Monitor - pg. 95
  - Lab 7-1: Heart Rate Sensor - pg. 96
  - Lab 7-2: Heart Rate Display - pg. 102

## Lab 7: Project

AJW

5/11/23

Heart Rate Monitor

## Equipment/Materials:

Part	Amt	Part	Amt	Part	Amt
74193	4	MCP6002	1	10kΩ Resistor	1
74192	2	7414	1	22kΩ Resistor	1
7-Seg	3	7404	1	Photo transistor NPN	1
7447	3	100k Trim Potentiometer	2	2N3904 NPN	1
0.01µF Cap	2	10k Trim Potentiometer	1	Buzzer	1
0.470µF Cap	1	1kΩ Resistor	2	555 Timer	2
47µF Cap		Super Bright LED	1	7408	1
22µF Cap		LED	1	7432	1
		220Ω Resistor	1	7476	1
		330Ω Resistor	1	330Ω Resistor Pack	3

Objectives:

1. Use knowledge acquired throughout this semester to design and construct a heart rate monitor.
2. Demonstrate the ability to find data sheets for new components, and use them to design my project.
3. Demonstrate the ability to <sup>AJW</sup> represent accurately analyze, predict and measure relevant values.
4. Demonstrate the ability to convert an analog input to a TTL input.

Theory of Operation

In this lab, I will be using everything that I have learned so far, to construct a heart rate monitor. In order to do this, I want to turn my heart rate into pulses on a square wave, which I can then use with counters to display my BPM (Beats per minute). To do this, I will be using an LED inside of a clip that goes on your finger, which will illuminate my finger with light. On the other part of the clip, will be a photo transistor, which will detect my pulse by detecting the change in light as my heart pumps blood through my finger.

## Lab 7: Project

AJW  
5/11/23

My approach to this will be a bit different compared to other labs, as I will have to play around, and try different things to find what works.

Figure 7-1-1: Heart Rate Sensor

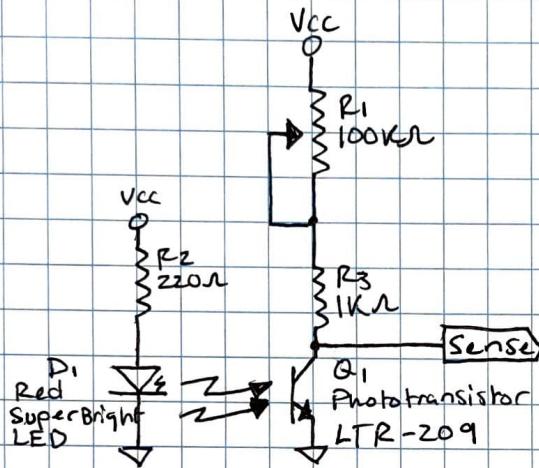


Table 7-1-1 LTR-209 Limitations	
Parameter	Value
Power Dissipation	100 mW
Collector Dark Current	100 nA
On State Collector current	4 mA
V <sub>CE</sub> Breakdown	30V
V <sub>EC</sub> Breakdown	0.4V

This is the circuit that I found worked the best for detecting my pulse with this phototransistor. I tried different colored LEDs, Infrared LEDs, and found that having the Red Superbright LED on your finger tip, with the transistor on the nail works the best. I have a 220 LED to give it a bit more current to make it brighter to give myself the best illumination. The 1kΩ resistor with a 100kΩ trim pot are to bias the transistor, so that I can tune it for the best signal out. The 1kΩ is mainly a current limiting resistor to make sure that the transistor is not out of spec, even if the rheostat is 0Ω.

I then need to amplify this  $V_{sense}$  as it only gave me around 50 mV out. So I will use an MCP6002 Op Amp. What I found with this however, is that I had a loading issue, resulting in no output from the amplifier, so to correct this, I had to use a voltage follower as a buffer to impedance match my input to the amp which has a high  $Z_{in}$ . Then I can put this amplified heart beat into a Schmitt trigger to give me a nice square wave output at 0V to 5V, and this will also help reduce any oscillations I might have from my signal.

## Lab 7: Project

AJW  
5/1/23

Now, when I built my amp, I found that I had some high frequency oscillations, so between my voltage follower,  $U_1$  and my amplifier, I made a low pass filter out of a  $10\text{k}\Omega$  resistor and a  $330\mu\text{F}$  capacitor, to filter anything above half of a Hertz. However, it took nearly 10 seconds to start giving you a signal for your heart beat, so I began experimenting by swapping the resistor for a  $1\text{k}\Omega$  one, and tried lower capacitance values. I ended up with a filter made up of a  $1\text{k}\Omega$  resistor and a  $47\mu\text{F}$  capacitor. It now takes about 2-3 seconds to give you a signal for the capacitor to adjust to the input of your finger. This doesn't give quite as clean of a signal but still works great with the Schmitt Trigger.

Figure 7-1-2: Amplifier Stage


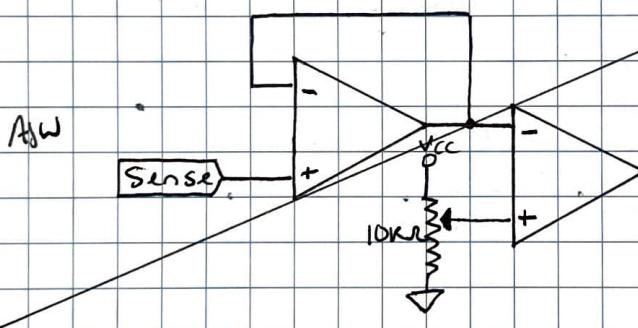


Figure 7-1-2i: Amplifier Stage

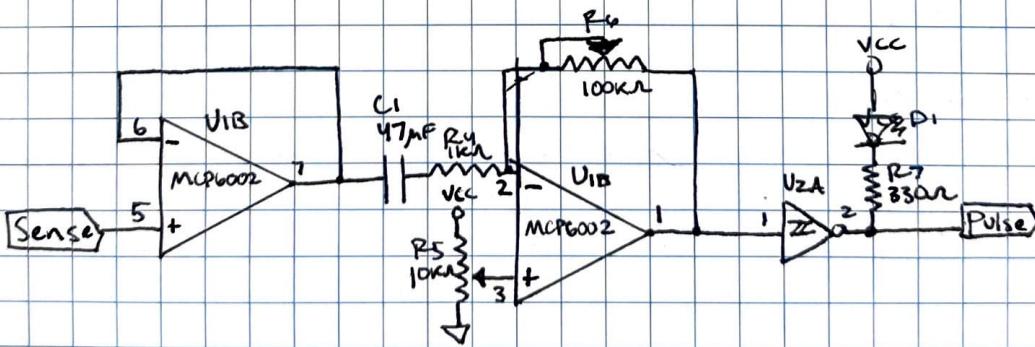

So this circuit will amplify my heart beat, and turn it into a square wave using the Schmitt trigger. With this, I hooked up an LED to the output of the trigger, and it will give us a normal low, lighting the LED, and a pulse will give me a high, turning it off every time that my heart beats, giving me a visual indicator, but also telling me if I have any oscillations by seeing it flicker when I do.

AJW  
5/1/23

## Lab 7: Project

AJW  
5/2/23

The potentiometers on the amplifier are used to tune the amplifier while the 10k (R<sub>S</sub>) sets my DC voltage or my zero point. And R<sub>b</sub>, the 100k is used to set my gain, I ended up just maxing it out to get the most out of it, this made it so that I could get a gain of around 100 with the 1k<sub>L</sub> resistor in there, and made it so I could amplify my  $\approx 50mV$  to about -5V, which is perfect for trying to make it a digital signal using my schmitt trigger. As well, with my V<sub>DD</sub> pin to V<sub>CC</sub> w/ 5V, it would make it clip at 5V, and 0V, due to V<sub>SS</sub> being to ground.

Calculations

Now that I have my base circuits, I want to find my Worst Case Loading Calculations so that I can ensure that everything is in spec.

Table 7-1-2: Loading Calcs for

Figure 7-1-1

AJW

Worst	V <sub>H</sub> , P <sub>in#</sub>	Value
V <sub>IL</sub>		
V <sub>IH</sub>		
I <sub>OL</sub>		
I <sub>O<sub>H</sub></sub>		

$$I_{CSAT}, R_L = 0\Omega$$

$$I_{CSAT} = V_{CC}/R_S$$

$$I_{CSAT} = 5V/1k\Omega$$

$$\boxed{I_{CSAT} = 5mA}$$

So with just a 1k<sub>L</sub> resistor, it would actually be out of spec, as it is more than the 4mA in the data sheet minimum Resistance. There should be at least 1.25k<sub>L</sub> to keep it in spec no matter what.

Table 7-1-2: Loading Calcs for

Figure 7-1-2

Worst	V <sub>H</sub> , P <sub>in#</sub>	Value
V <sub>IL</sub>	U <sub>2A</sub> , 1	0.4V
V <sub>IH</sub>	U <sub>2A</sub> , 1	5V
I <sub>OL</sub>	U <sub>2A</sub> , 2	7.879mA
I <sub>O<sub>H</sub></sub>	U <sub>2A</sub> , 2	0A

$$I_{OL} = (V_{CC} - V_D - V_{OL}) / R_L$$

$$I_{OL} = (5V - 2V - 0.4V) / 1330\Omega$$

$$\boxed{I_{OL} = 7.879mA}$$

# Lab 7: Project

AJW  
5/12/23


Now, I want to hook up a buzzer, to beep as your heart beeps, so I want to beep it on a high. However, it requires a lot of current (over 20mA), so I need to create a driver using a transistor. However, I also don't want it to beep for an extended period of time if left saturated, so I need to come up with some logic to prevent it from constantly buzzing.

AJW  
5/14/23  
10:45

This was the idea that we had come up with for this purpose.


AJW  
5/14/23  
10:00

Figure 7-1-3: Buzzer Circuit V1:

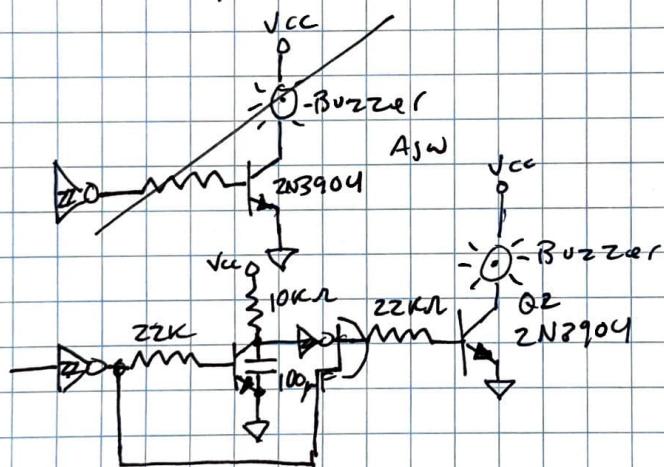

The idea with this circuit was to drive the buzzer, but if left saturated for too long, then it would turn off the buzzer, so if anything happened, then it would turn off after a few seconds. However, it didn't really discharge fast enough to work and charge quick enough to beep it properly. Plus, it also made it always give off this sort of squeal, so we scrapped that and just used a single driver with no cap, because it didn't work like we wanted it to anyways. So this was the circuit that I soldered onto my board.

Figure 7-1-4: Buzzer Circuit V2

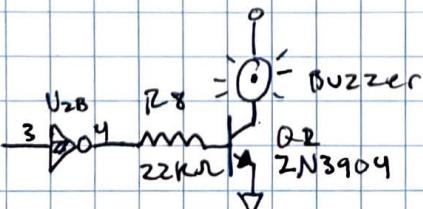

AJW  
5/14/23

## Lab 7 - Project

AJW  
5/14/23

for this circuit, the buzzer wants a lot of current, so that is why I had to use a driver for it, to not damage my TTL components. And I had to make sure to keep  $I_B$  high to keep  $I_C$  high. For that, I want to keep it saturated when the output of my schmitt trigger goes high.

$$I_B = (V_{OH} - V_{BE}) / R_B$$

$$I_B = (4V - 0.7V) / 22k$$

$$\boxed{I_B = 150\mu A}$$

$$I_C = I_B \cdot \beta$$

$$I_C = 150\mu A \cdot 200$$


$$\boxed{I_C = 30mA}$$

It's hard to say what my  $I_{Csat}$  is, as I don't have any specs for the buzzer.

Measurements

In order to measure this circuit, I had to tune it. To do this, I adjusted my potentiometers while looking at the output of the collector, and both the input and output of the schmitt trigger. I tuned the first 100kΩ one to bias the photo transistor, and get the highest output of it. The 2nd 100kΩ was adjusted to get the most gain that I could. And the 10kΩ was to adjust the input voltage for the amplifier, and adjust the DC level of my output.

I then used the LED as an indicator as to whether or not I was getting a clear signal. This circuit is pretty touchy and there are so many things outside of the circuit that affect it.

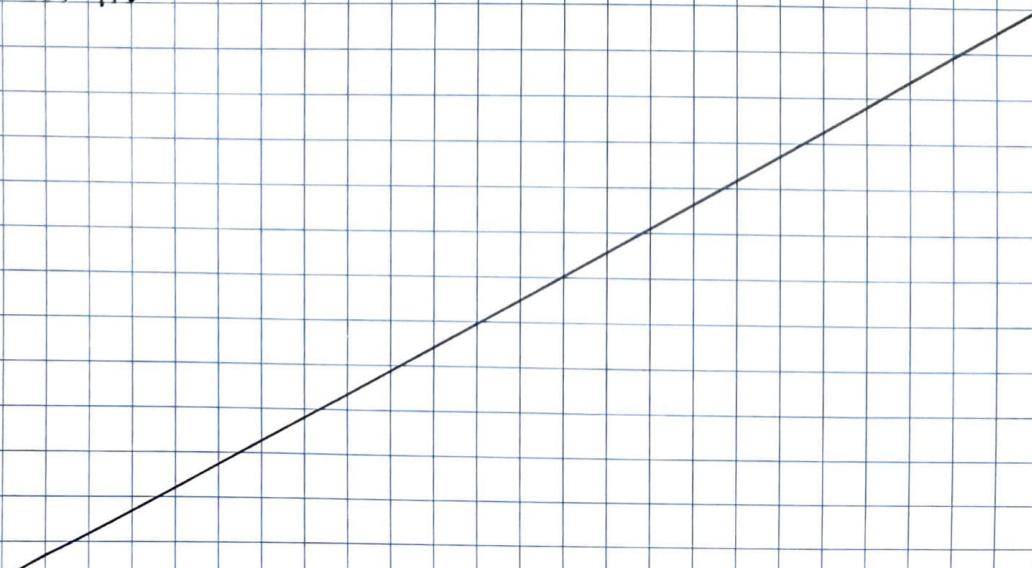AJW  
5/14/23

AJW  
5/4/23

Project 7:

Lap 7 - Project

Waveforms/Diagrams

Figure 7-1-5: Measured Collector Output


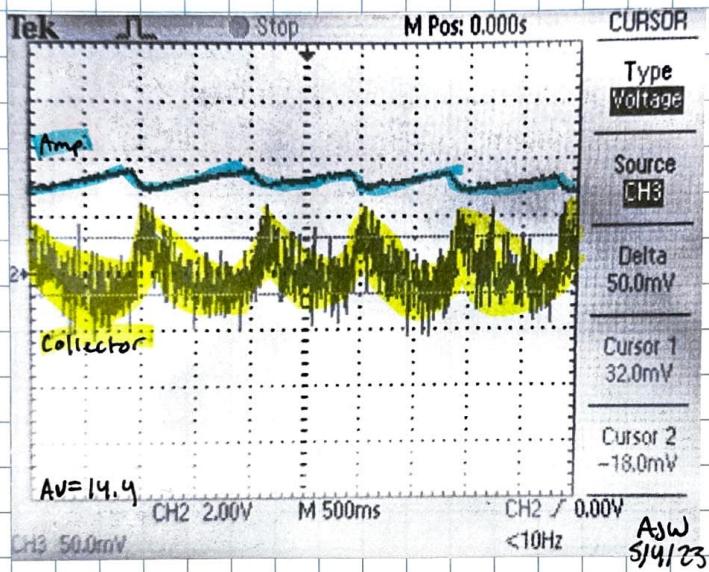


Figure 7-1-6: Measured Amplifier Output

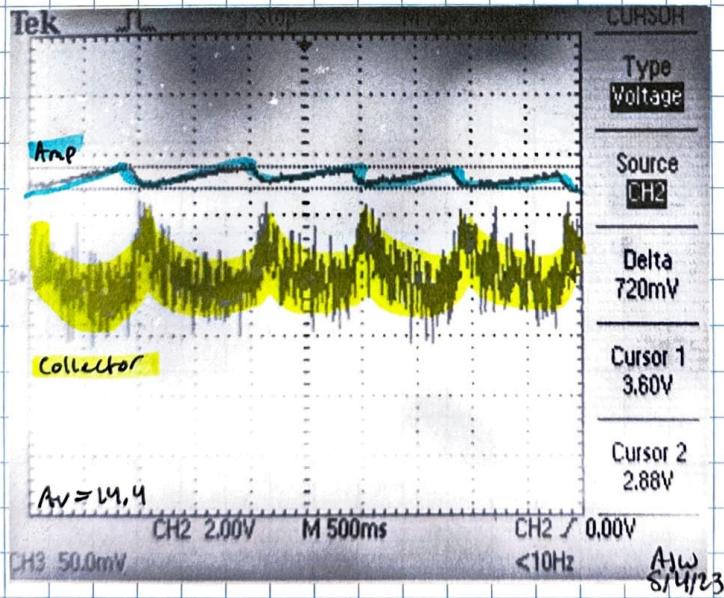

These show that I was able to get my heartbeat using this circuit, but you could get more or less depending on whether or not you were stationary, or how good of a position your finger was in.

AJW  
5/4/23

AW  
SM123Theory of Operation

In this section, I will cover the display circuit that I was going to use for my sensor, to display the beats per minute of the person with their finger in the sensor.

To solve this problem, we first tried a circuit that counted in 10ms intervals, the time between heartbeats. This didn't work, because we could set it to be spot on at one interval, but it would get exponentially further away from the actual value due to the non-linearity of heart beats and frequency of beats.

We looked up solutions in books, and then online for how to convert hex to or binary to BCD, in order to hook it up to our 7-Segment Displays. We eventually found a solution, but did not have the time to test and/or implement it.

The idea was that we were going to use one set of counters to count the amount of heart beats in 7.5 seconds, and then count down the amount of beats times 8, by shifting the input by 3 bits. We would count down to zero, and then at the same time, count up on a set of BCD counters. So we were counting down in decimal, the exact amount of times that we are counting up in BCD, essentially converting it so that we can display the BCD number on our 7-segment displays. This circuit has a lot going on, and because of that, didn't have the time to make sure it worked or solder it.

In case I eventually return to this circuit, or someone picks up from my place to improve/finish it, I will still be going over it.

Calculations

The first things that I want to calculate are my clock sources, for 7.5s and 1KHz

AW  
SM123

## Lab 7-2: Display Circuit

AJW  
5/14/237.5s:

$$R_A = \frac{+}{-C(\ln(\frac{V_C - V_F}{V_i - V_F}))}$$

$$R_A = \frac{15s}{2\pi f (\ln(\frac{3.333 - 5}{1.667 - 5}))}$$

$$R_A = 984.082 \text{ k}\Omega$$

50% Duty Cycle:

$$R_B = 10 \cdot R_A$$

$$R_B = 10/11 \cdot R_T$$

$$R_B = 10/11 \cdot 984.082 \text{ k}\Omega$$

$$R_B = 899.67 \text{ k}\Omega$$

$$R_A = 89.462 \text{ k}\Omega$$

$$R_B = 910 \text{ k}\Omega$$

$$R_A = 91 \text{ k}\Omega$$

1kHz:

$$T = f^{-1}$$

$$T = fK^{-1}$$

$$T = 1 \text{ ms}$$

$$1/3T = 333.333 \mu\text{s}$$

$$R = \frac{+}{-C(\ln(\frac{V_C - V_F}{V_i - V_F}))}$$

$$R = \frac{333.333 \text{ ms}}{400 \text{ nF} (\ln(\frac{1.667 - 0}{3.333 - 0}))}$$

$$R = 1.024 \text{ k}\Omega$$

$$R = 1 \text{ k}\Omega$$

As that 7.5 second clock makes your circuit accurate or not, you want to be as close to that 7.5s as possible, so you can put a 100kΩ rheostat or something between the cap and RB to adjust/fine tune it.

I also only want to count in that 7.5s that it is low, so during the pulse width, so I will OR the Pulse input with it to only count during the low pulse width.

As well, I will want an edge trigger for my Clear on the first input and Load on the second set of counters. So I will have two edge triggers, but the clear one will need to be buffered first so that we can load and start counting down before clearing the first set of counters.

Then I will need to come up with the logic for making my 3rd set of counters count, and stop counting,

AJW  
5/14/23

104


## Lab 7-2: Display circuit

AJW  
5/4/23Table 7-2-1: Truth Table  
for 3rd set of counters

A	B	Count
0	0	Unused
0	1	1 stop count
1	0	0 Count
1	1	Unused

Table 7-2-1: Loading Calcs  
for Display Circuit


Worst	U <sub>H</sub> , P <sub>int</sub>	Value
V <sub>IL</sub>	U <sub>OA</sub> , 1	5V
V <sub>IL</sub>	U <sub>3</sub> , 5	0.9V
I <sub>OH</sub>	U <sub>UD</sub> , 8	80μA
I <sub>OL</sub>	U <sub>UD</sub> , 8	3.2mA

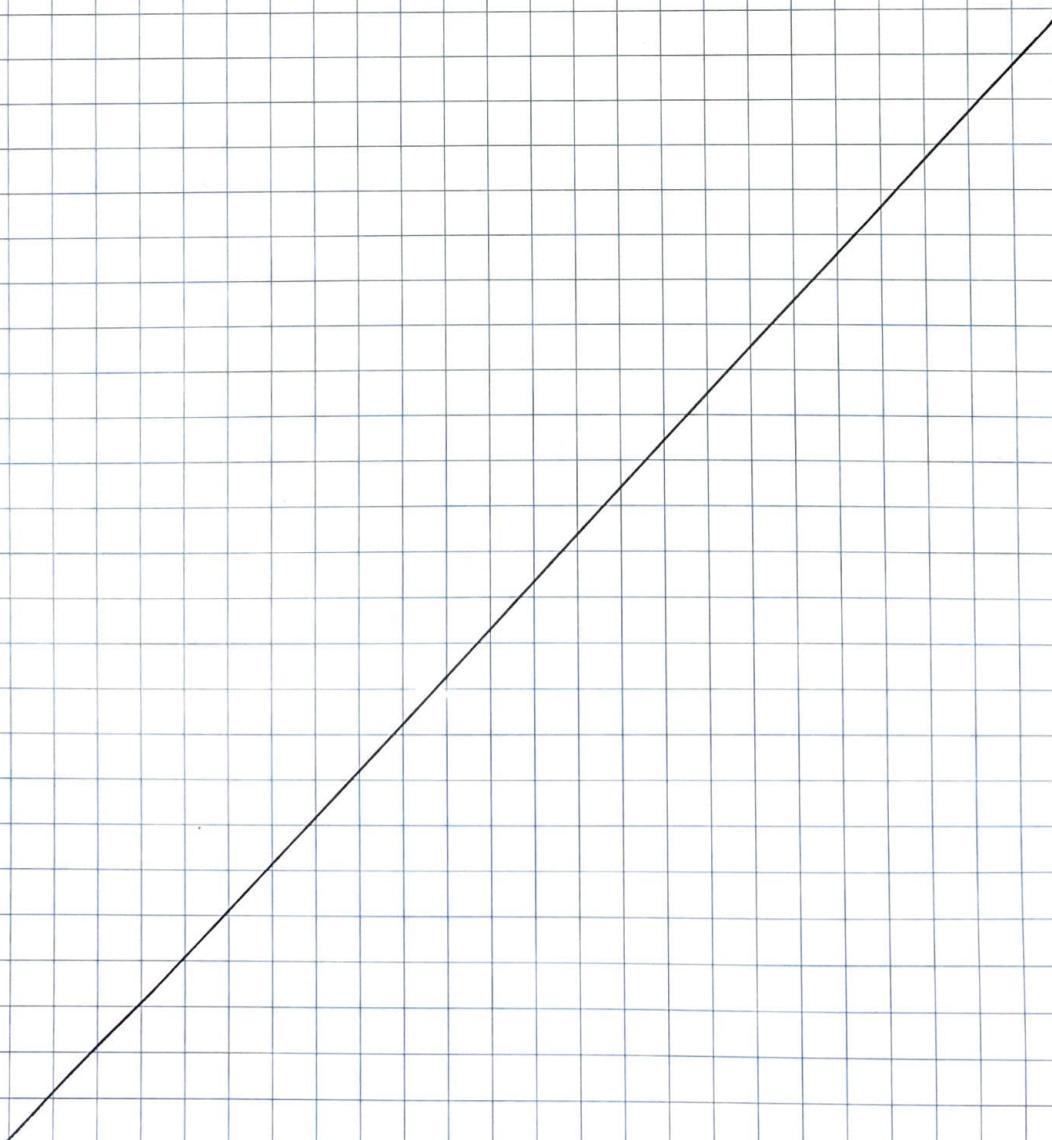AJW  
5/4/23

## Lab 7-2: Display Circuit


AJW  
5/8/23

Figure 7-2-1: Display Circuit for Heart Beat Monitor

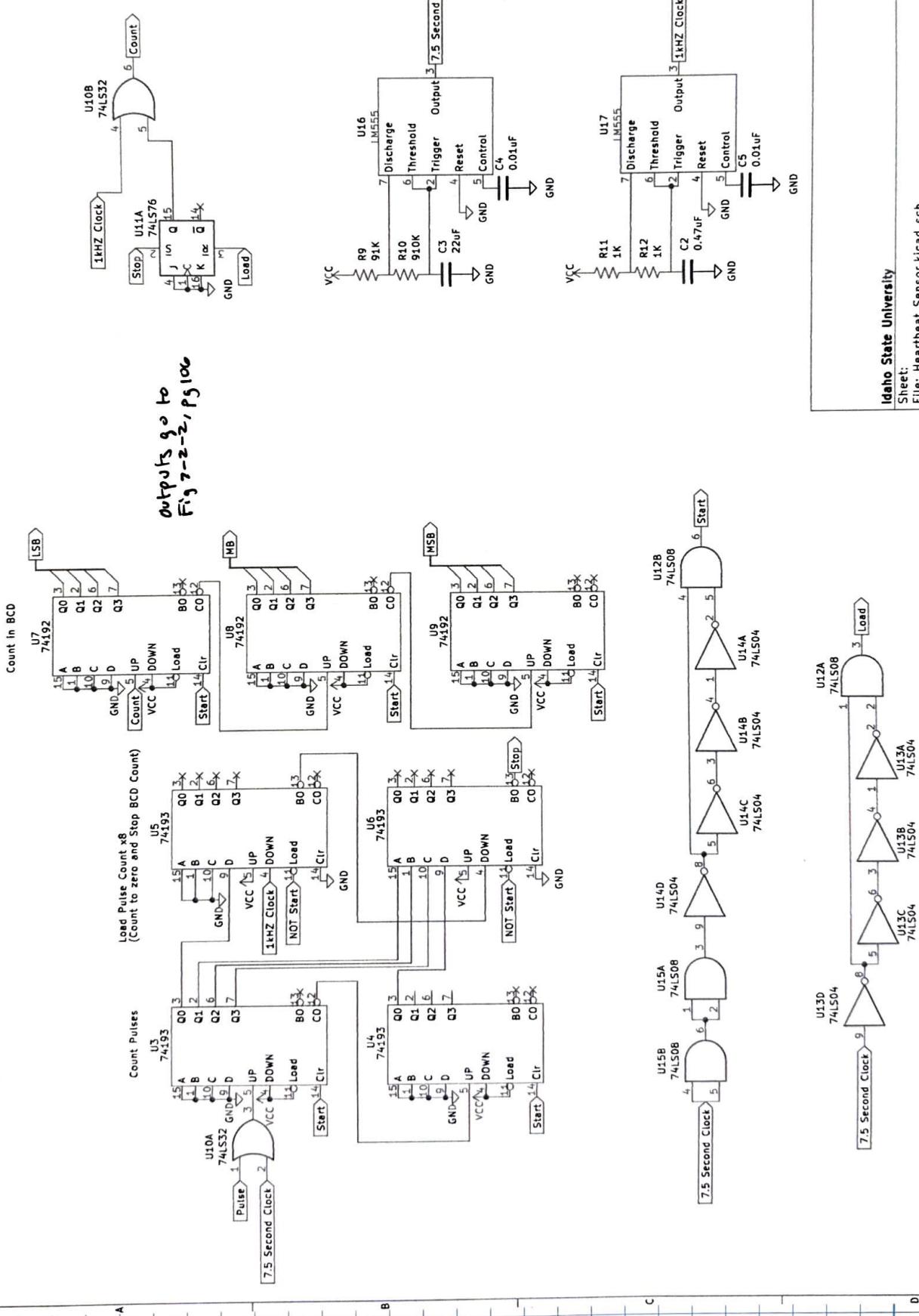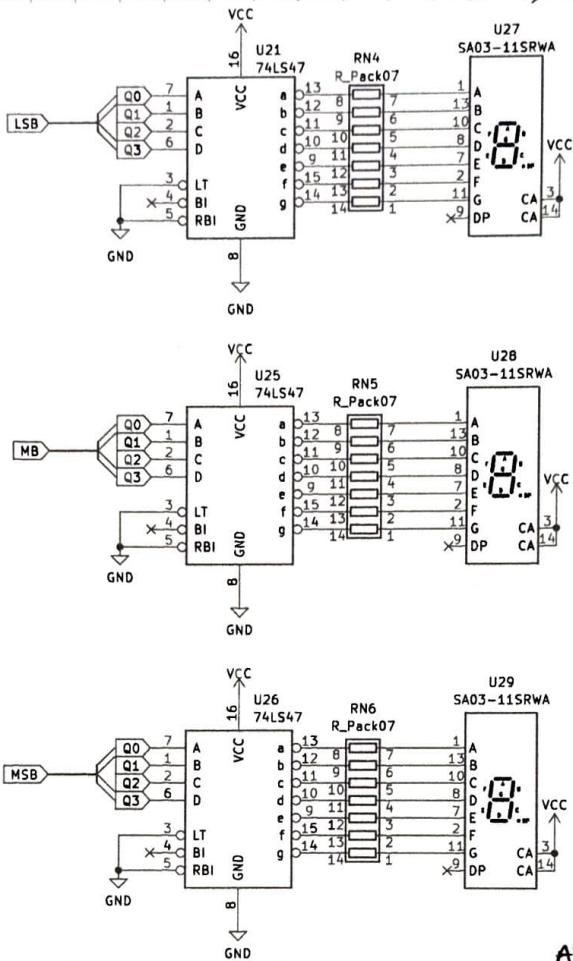AJW  
5/8/23AJW  
5/8/23

AW  
8/8/23

Figure 7-2-2: 7-Segment Display Circuit

AW  
8/8/23Conclusion

This project was very cool, not only was it challenging trying to use new components, but it was fun applying what I have learned to try and build something with it. There were many challenges with this circuit and plenty of troubleshooting, and time spent working things out on the whiteboard.

I am not entirely satisfied with the end product of this project regarding the stability of it. It is very sensitive to even the slightest of movement. As well, the clip that goes on your finger is something that I struggled with. You need very precise placement in order to get a good signal from it. If I had more time, I would try adjusting the amount of tension on the finger from the spring of the clip. As well, I would finish the display circuit, as it would be much more complete if it told you your heart rate. If I ever get the chance, I would like to finish it, but I

AW  
8/8/23

## Lab 7-2: Display Circuit

AJW  
5/5/23

believe that overall, I have laid down a very good foundation for someone to build upon/improve. With the main thing being the stability to be improved.

I think that I covered a lot of ground in the time that I worked on this project, starting from scratch basically. An idea that may make the stability better would be 3D printing a new clip, as another problem is the narrow angle of the photo transistor, and trying to improve that in some way.

If I ever return to this project, or someone else picks it up, I am sure that they or I can make it better with what I have learned.

And by doing complex things with these basic components, makes me realize how amazing micro-controllers are, and how they make the possibilities so much better for things you can do. As this would've been much more simple, especially with the display part of it with one

Kyle W. 5/5/23

TJF  
5-5-23